

EC2.101 – Digital Systems and Microcontrollers

Practice Sheet 2 (Lec9– Lec 12)

Q1. A 4-variable function $F(w, x, y, z)$ has minterms $m_3, m_4, m_5, m_7, m_9, m_{13}, m_{14}, m_{15}$ find the simplified boolean expression for the function.

Q2. Minimize the following expression using K-map.

$$Y = \sum m(0, 1, 5, 9, 13, 14, 15) + \sum d(3, 4, 7, 10, 11)$$

Q3. Solve the kmap for

1. $F(x, y, z) = \prod M(0, 5)$
2. $F(x, y, z) = \sum m(1, 2, 3, 4, 6, 7)$

Q4. Solve for 5 variables kmap

$$F(a, b, c, d, e) = ab'cd + a'b'cde + ab'c'de + a'bcde$$

Q5. Implement the following gates using a 2-to-1 multiplexer.

1. 2 input AND gate
2. 2 input XOR gate

Q6 Implement 4-to-1 mux using 2-to-1 multiplexers.