

# Mid Semester Exam – Solutions

**Q1. [4 marks for the Equations, 3 marks for process and solving, 3 marks for final condition and answer] OR [7 marks for Truth Table, 3 marks for final condition and answer]**

- Assume Truth = 1, Lying = 0.
- Assume
  - A = Statements made by Abdul
  - B = Statements made by Bishnoi
  - C = Statements made by Carren
  - D = Statements made by David
- Given,
  - $A' = B + C'$
  - $B' = A' + D$
  - $C = A$
  - $D = A'B' + C'$
- The requirement is to find when all these conditions are simultaneously true. Substituting the third statement into first,

$$\Rightarrow A' = B + A'$$

- If  $B = 0$ ,

$$\Rightarrow A' = 0 + A'$$

$$\Rightarrow A' = A'$$

which is always true.

- If  $B = 1$ ,

$$\Rightarrow A' = 1 + A'$$

$$\Rightarrow A' = 1$$

which *need not* always be true.

- Hence,  $B = 0$ . Substituting this into the fourth statement,

$$D = 0 + C'$$

$$\Rightarrow D = C' = A'$$

- Substituting into the second statement,

$$\Rightarrow 1 = A' + A'$$

$$\Rightarrow A' = 1$$

$$\Rightarrow D = 1, C = 0$$

- Therefore,

$$A = 0, B = 0, C = 0, D = 1$$

- David is telling the truth.

**Q2.**

- The output is correct only for the highlighted entries truth table, as given in the question.


$B_1$	$B_0$	$A_1$	$A_0$	$C_3$	$C_2$	$C_1$	$C_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

**[2 Marks for the Truth Table]**

- We can clearly see that the product  $A_1B_0$  is 1 in the correct cases *and* it is zero everywhere else.

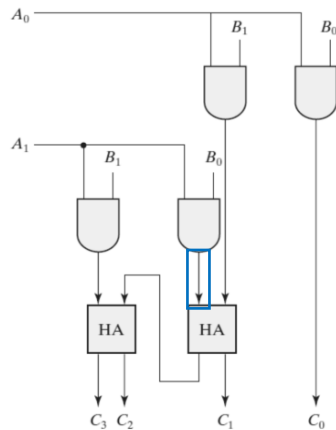**[7 Marks if the pattern is identified]**

- Additionally, it is the output wire of one of the AND gates in the circuit as highlighted below.




- If that wire is stuck at VDD and everything else in the circuit was operating as it should, we will observe the specified case in the question.
- Hence, the output wire of the AND gate with inputs  $A_1$  and  $B_1$  is problematic, and it is stuck at VDD.

**[10 Marks for full solution]**

**Q3.**

**Part 1(5 Marks)**

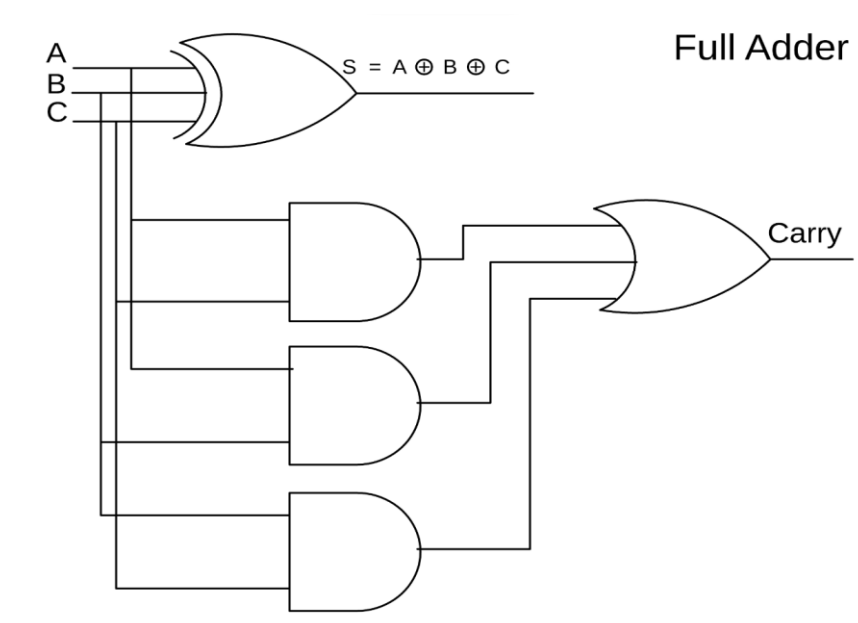

$$sum = A \oplus B \oplus C$$

$$carry = AB + BC + AC$$

**[2 Marks for expressions]**

for  $sum = A \oplus B \oplus C$  we need 3 input xor gate which can be realised with 2 xor gates

for sum we need 16\*2 Transistors

for carry  $AB + BC + AC$  we need 3 - 2 input OR gates and 1 -3 input or gate

for carry we need 6\*3 T+ 8\*1 T

so for 1 full adder we need 58 transistors

As it is cascaded n bit adder we need 58n transistors

**[3 Marks for calculation and final answer]**

## Part 2

For CLA Adder

$$P_i = A_i \oplus B_i$$

$$G_i = A_i . B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

**[2 Marks for expressions]**

$$C_1 = G_0 + P_0 C_{in}$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_{in}$$

$$C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{in}$$

So on

So for computing  $c_i$  using  $G_i, P_i$

$c_1$  we need 6 transistors for AND ,6 transistors for OR gate =12T

$c_2=6$  for 2 input AND gate, 8 for 3 input AND gate and 8 for 3 input OR gate=22T

$$c_3 = 6 + 8 + 10 + 10 = 34T$$

$$C_n = n^2 + 7n + 4$$

For computing S we need 2 input XOR gate that is 16 transistors

For computing  $P_i$  we need 2 input XOR gate that is 16 transistors

For computing GI we need 2 input AND gate that is 6 transistors

$$\text{Total count} = \sum C_i + 38 = \sum i^2 + 7i + 4 + 38 = \frac{n(2n+1)(n+1)}{6} + 7 \frac{n(n+1)}{2} + 4n + 38n$$

$$= \frac{1}{3}n^3 + 4n^2 + \frac{11}{3}n + 42n = \frac{1}{3}n^3 + 4n^2 + \frac{137}{3}n$$

**[3 Marks for calculation and final answer]**

**Q4.**

- It is given in the question that  $aabb$  is a perfect square and a decimal number.

$$aabb = 10^3a + 10^2a + 10b + b$$

$$= 10^2a(10 + 1) + 11b$$

$$= 11(10^2a + b)$$

- For the above quantity to be a perfect square,  $(10^2a + b)$  should be divisible by 11 and the quotient should be a perfect square, i.e.

$$(10^2a + b) = 11n^2$$

**[2 Marks till here] - So if guessing starts here and concludes in right answer, 3 Marks (No extra mark if final answer is wrong).**

- Since  $a, b \in \mathbb{Z}^+$  and  $a, b \in [0, 9]$ ,

$$10a^2 + b = (a0b)_{10}$$

- The divisibility rule of 11 dictates that the quantity  $(a + b - 0)$  should be zero or divisible by 11. Since the former is not possible, and  $a, b \in [0, 18]$ ,

$$a + b = 11$$

**[4 Marks till here] - If guessing starts here and concludes in right answer, 6 Marks (No extra mark if final answer is wrong).**

- Performing the division,

$$\begin{array}{r} 11 \overline{) a \ 0 \ b \ x} \\ \underline{x \ x} \end{array}$$

- The remainder contains two digits  $(a - 1 - x)$ , and  $(10 - x)$ . The remainder should also  $\in [0, 10]$ , because we are dividing with 11.

$$\Rightarrow a - 1 - x = 1 \text{ **AND** } 10 - x = 0$$

(OR)

$$a - 1 - x = 0, \text{ in which case the second digit } \in [0, 9]$$

- The first condition above leads to  $a = 13$ , which is a contradiction.

$$\Rightarrow a = x + 1$$

- Now, continuing the division

$$\begin{array}{r} 11 \overline{) a \ 0 \ b \ [ \ xy} \\ \underline{x \ x} \phantom{b} \\ (10 - x) \ b \\ \phantom{(10 - x)} y \phantom{b} \end{array}$$

$$\Rightarrow 10 - x = y \text{ **AND** } b = y$$

(OR)

$$\Rightarrow 9 - x = y \text{ **AND** } b + 10 = y$$

- Expanding the first condition,

$$\Rightarrow b = 10 - x$$

$$\Rightarrow a + b = 10 - x + x + 1 = 11$$

which is true. Therefore,

$$a = x + 1 \Rightarrow x = a - 1$$

$$b = y = 10 - x$$

$$\Rightarrow y = 10 - a + 1 = 11 - a$$

- The final condition is that  $(xy)_{10}$  should be a perfect square.

$$(xy)_{10} = 10(a - 1) + 11 - a$$

$$= 9a + 1$$

$$\Rightarrow 9a + 1 = n^2$$

**[7 Marks till here] – If guessing starts here and concludes in right answer, 8 Marks (No extra mark if final answer is wrong).**

Since  $a \in [0, 9]$  and  $a \in \mathbb{Z}^+$

$$\Rightarrow n^2 \in [1, 82]$$

$$\Rightarrow n \in [1, 9] \text{ and } n \in \mathbb{Z}^+$$

Now

$$a = \frac{n^2 - 1}{9}$$
$$= \left(\frac{n-1}{3}\right)\left(\frac{n+1}{3}\right)$$

For  $a \in \mathbb{Z}^+$ , both  $n-1$  and  $n+1$  should be divisible by 3. However,  $n-1$ ,  $n$ ,  $n+1$  are consecutive integers. Hence, if  $n-1$  is divisible by 3,  $n+1$  is not – and vice versa. The only possibility for  $a \in \mathbb{Z}^+$  is if either  $n-1$  or  $n+1$  is equal to 9 (Multiple of 9 is also enough, but  $n \in [1, 9]$ ).

$$\Rightarrow n = 8$$

$$\Rightarrow a = 7$$

$$\Rightarrow b = 4$$

Therefore, the original decimal number is **7744**.

**[10 Marks for full solution]**